

模組表示法

- HDL 範例3 -1

//Description of the simple circuit of Fig. 3-37

```
module smpl_circuit(A,B,C,x,y);
```

```
  input A,B,C;
```

```
  output x,y;
```

```
  wire e;
```

```
  and g1(e,A,B);
```

```
  not g2(y, C);
```

```
  or g3(x,e,y);
```

```
endmodule
```

 


Fig. 3-37 Circuit to Demonstrate HDL

閘延遲

- HDL 範例 3-2

//Description of circuit with delay

```
module circuit_with_delay (A,B,C,x,y);  
  input A,B,C;  
  output x,y;  
  wire e;  
  and #(30) g1(e,A,B);  
  or #(20) g3(x,e,y);  
  not #(10) g2(y,C);  
endmodule
```

HDL 範例 3-3

(模擬一個具有延遲電路的測試平台)

```
//Stimulus for simple circuit
```

```
module stimcrct;
```

```
reg A,B,C;
```

```
wire x,y;
```

```
circuit_with_delay cwd(A,B,C,x,y);
```

```
initial
```

HDL 範例 3-3

(模擬一個具有延遲電路的測試平台)

begin

A = 1'b0; B = 1'b0; C = 1'b0;

#100

A = 1'b1; B = 1'b1; C = 1'b1;

#100 **\$finish**;

end

endmodule

HDL 範例 3-3

(模擬一個具有延遲電路的測試平台)

```
//Description of circuit with delay
module circuit_with_delay (A,B,C,x,y);
    input A,B,C;
    output x,y;
    wire e;
    and #(30) g1(e,A,B);
    or #(20) g3(x,e,y);
    not #(10) g2(y,C);
endmodule
```

布林表示式

$$x = A + BC + B'D$$

$$y = B'C + BC'D'$$

- HDL 範例 3-4

//Circuit specified with Boolean equations

```
module circuit_bln (x,y,A,B,C,D);
```

```
    input  A,B,C,D;
```

```
    output x,y;
```

```
    assign x = A | (B & C) | (~B & C);
```

```
    assign y = (~B & C) | (B & ~C & ~D);
```

```
endmodule
```

使用者定義的原始值

- 使用關鍵字 `primitive` 作宣告
- 只可以有一個輸出且此輸出必須列在埠名單的第一個還有必須用關鍵字 `output` 來宣告。
- 輸入數目不限制，至於它們在 `input` 宣告中的順序則必須與它們在下面表中所給值的順序相同。

使用者定義的原始值(UDP)

- 真值表必須在關鍵字table及endtable之間。
- 輸入值依順序列出，用冒號(:)代表結束，輸出通常是每一列的最後一個記錄，後面跟著是一個分號(;)。
- 最後用關鍵字endprimitive作結束。

HDL 範例 3-5

(利用一個真值表來定義UDP)

//User defined primitive(UDP)

primitive crctp (x,A,B,C);

output x;

input A,B,C;

//Truth table for $x(A,B,C) = \text{Minterms } (0,2,4,6,7)$

table

HDL 範例 3-5

(利用一個真值表來定義UDP)

```
// A B C : x (Note that this is only a comment)
  0 0 0 : 1;
  0 0 1 : 0;
  0 1 0 : 1;
  0 1 1 : 0;
  1 0 0 : 1;
  1 0 1 : 0;
  1 1 0 : 1;
  1 1 1 : 1;

endtable
endprimitive
```

HDL 範例 3-5

(利用一個真值表來定義UDP)

```
//Instantiate primitive  
module declare_crctp;  
    reg x,y,z;  
    wire w;  
    crctp (w,x,y,z);  
endmodule
```