

4-11 組合電路的硬體描述語言

□ 閘階層模型

關鍵字 and、nand、or、nor、xor、xnor、not、buf

表 4-9 預先定義原始閘的真值表

and	0	1	x	z	or	0	1	x	z
0	0	0	0	0	0	0	1	x	x
1	0	1	x	x	1	1	1	1	1
x	0	x	x	x	x	x	1	x	x
z	0	x	x	x	z	x	1	x	x

xor	0	1	x	z	not	輸入	輸出
0	0	1	x	x		0	1
1	1	0	x	x		1	0
x	x	x	x	x		x	x
z	x	x	x	x		z	x

HDL 範例 4-1

(2對4線解碼器的閘階層描述)

//Gate-level description of a 2-to-4-line decoder

//Figure 4-19

```
module decoder_gl (A,B,E,D);
```

```
  input A,B,E;
```


```
  output [0:3]D;
```

```
  wire Anot,Bnot,Enot;
```

```
  not
```

```
    n1 (Anot,A),
```

```
    n2 (Bnot,B),
```

 

HDL 範例 4-1

(2對4線解碼器的閘階層描述)

n3 (Enot,E);

nand

n4 (D[0],Anot,Bnot,Enot),

n5 (D[1],Anot,B,Enot),

n6 (D[2],A,Bnot,Enot),

n7 (D[3],A,B,Enot);

endmodule

HDL 範例 4-2

(4位元加法器之底部向上層次化描述)

```
//Gate-level hierarchical description of 4-bit  
  adder  
  
// Description of half adder (see Fig 4-5b)  
module halfadder (S,C,x,y);  
  input  x,y;  
  output S,C;  
  
//Instantiate primitive gates  
  xor (S,x,y);  
  and (C,x,y);
```

HDL 範例 4-2

(4位元加法器之底部向上層次化描述)

```
endmodule
```

```
//Description of full adder (see Fig 4-8)
```

```
module fulladder (S,C,x,y,z);
```

```
    input  x,y,z;
```

```
    output S,C;
```

```
    wire  S1,D1,D2;
```

```
//Outputs of first XOR and two AND gates
```

```
//Instantiate the halfadder
```

```
    halfadder HA1 (S1,D1,x,y),
```

HDL 範例 4-2

(4位元加法器之底部向上層次化描述)

```
            HA2 (S,D2,S1,z);
    or g1(C,D2,D1);
endmodule

//Description of 4-bit adder (see Fig
4-9)

module _4bit_adder (S,C4,A,B,C0);
    input [3:0] A,B;
    input C0;
```

HDL 範例 4-2

(4位元加法器之底部向上層次化描述)

```
output [3:0] S;  
output C4;  
wire C1,C2,C3; //Intermediate carries  
//Instantiate the fulladder  
fulladder FA0 (S[0],C1,A[0],B[0],C0),  
            FA1 (S[1],C2,A[1],B[1],C1),  
            FA2 (S[2],C3,A[2],B[2],C2),  
            FA3 (S[3],C4,A[3],B[3],C3);  
endmodule
```

三態閘

 
 
 
 


Fig. 4-31 Three-State Gates

bufif1 (OUT, A, control);
notif0 (Y, B, enable);

具有三態緩衝器之2對1線多工器

 


Fig. 4-32 2-to-1-Line Multiplexer with Three-State Buffers

```
module muxtri (A, B, select, OUT);  
  input A, B, select;  
  output OUT;  
  tri OUT;  
  bufif1 (OUT, A, select);  
  bufif0 (OUT, B, select);  
endmodule
```

資料流程模型

□ Verilog HDL運算子

表 4-10 Verilog HDL 運算子

符號	運算
+	binary addition ; 二進位加法
-	binary subtraction ; 二進位減法
&	bit-wise AND ; 位元的及運算
	bit-wise OR ; 位元的或運算
^	bit-wise XOR ; 位元的互斥或運算
~	bit-wise NOT ; 位元的反相運算
==	equality ; 全等
>	greater than ; 大於
<	less than ; 小於
{ }	concatenation ; 連結
?:	conditional ; 條件式

HDL 範例 4-3

(2對4線解碼器的資料流程描述)

```
//Dataflow description of a 2-to-4-line  
decoder
```

```
//See Fig.4-19
```

```
module decoder_df (A,B,E,D);
```

```
  input  A,B,E;
```

```
  output [0:3] D;
```

```
  assign D[0] = ~(~A & ~B & ~E),
```

```
          D[1] = ~(~A & B & ~E),
```

```
          D[2] = ~(A & ~B & ~E),
```

```
          D[3] = ~(A & B & ~E);
```

```
endmodule
```

HDL 範例 4-4

(4位元加法器之資料流程描述)

//Dataflow description of 4-bit adder

```
module binary_adder (A,B,Cin,SUM,Cout);
```

```
    input [3:0] A,B;
```

```
    input Cin;
```

```
    output [3:0] SUM;
```

```
    output Cout;
```

```
    assign {Cout,SUM} = A + B + Cin;
```

```
endmodule
```

HDL 範例 4-5

(大小比較器之資料流程描述)

//Dataflow description of a 4-bit comparator.

```
module magcomp (A,B,ALTB,AGTB,AEQB);
```

```
    input [3:0] A,B;
```

```
    output ALTB,AGTB,AEQB;
```

```
    assign ALTB = (A < B),
```

```
           AGTB = (A > B),
```

```
           AEQB = (A == B);
```

```
endmodule
```

HDL 範例 4-6

(2對1線多工器使用條件式運算子描述)

```
//Dataflow description of 2-to-1-line  
multiplexer
```

```
module mux2x1_df (A,B,select,OUT);
```

```
  input  A,B,select;
```

```
  output OUT;
```

```
  assign OUT = select ? A : B;
```

```
endmodule
```

行為模型

- HDL 範例 4-7
(2對1線多工器使用條件式運算子描述)

//Behavioral description of 2-to-1-line multiplexer

```
module mux2x1_bh(A,B,select,OUT);
```

```
    input A,B,select;
```

```
    output OUT;
```

```
    reg OUT;
```

```
    always @ (select or A or B)
```

```
        if (select == 1) OUT = A;
```

```
        else OUT = B;
```

```
endmodule
```

HDL 範例 4-8 (4對1線多工器之行為描述)

```
//Behavioral description of 4-to-1- line  
multiplexer  
//Describes the function table of Fig. 4-25(b).  
module mux4x1_bh (i0,i1,i2,i3,select,y);  
    input i0,i1,i2,i3;  
    input [1:0] select;  
    output y;  
    reg y;
```

HDL 範例 4-8

(4對1線多工器之行為描述)

```
always @ (i0 or i1 or i2 or i3 or select)
```

```
    case (select)
```

```
        2'b00: y = i0;
```

```
        2'b01: y = i1;
```

```
        2'b10: y = i2;
```

```
        2'b11: y = i3;
```

```
    endcase
```

```
endmodule
```

測試平台

- 一個模擬模組是具有下列形式的HDL程式

module 測試名稱。

宣告特有的reg和wire識別字。

在測試下列示設計模組。

利用initial及always敘述產生模擬。

顯示輸出響應。

endmodule。

系統功能

- **\$ display**-- 顯示具有 end-of-line return之變數或字串的一次值。
 - **\$write**—與 **\$display**相同，但是沒有到下一行。
 - **\$monitor**—當在模擬期間值改變時及顯示變數。
 - **\$time**--顯示模擬時間。
 - **\$finish**--結束模擬。
-

模擬與設計的交互模組

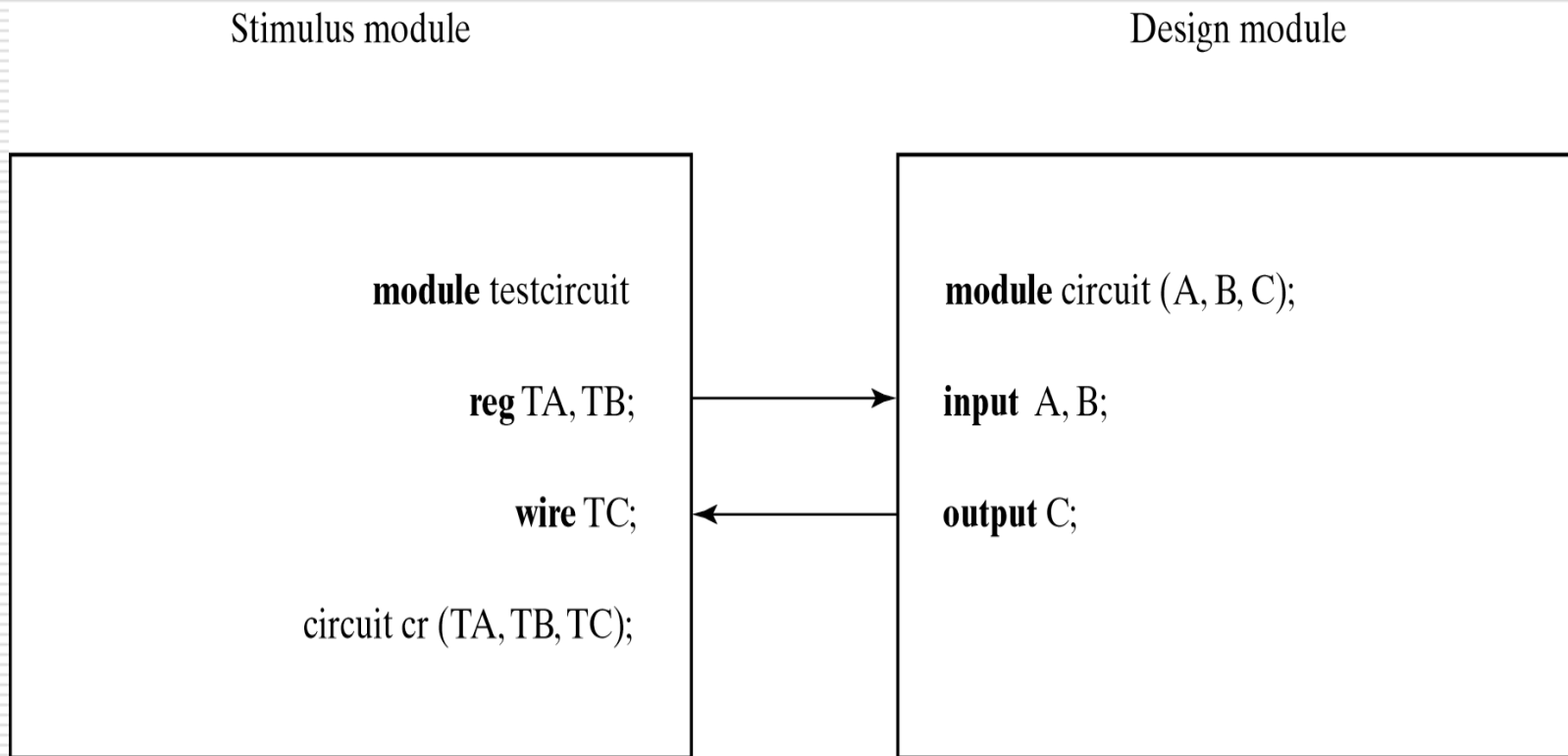


Fig. 4-33 Stimulus and Design Modules Interaction

HDL 範例 4-9

(測試範例4-6所描述的2對1多工器)

```
//Stimulus for mux2x1_df.
```

```
module testmux;
```

```
    reg TA,TB,TS; //inputs for mux
```

```
    wire Y;      //output from mux
```

```
    mux2x1_df mx (TA,TB,TS,Y);
```

```
// instantiate mux
```

```
    initial
```

HDL 範例 4-9

(測試範例4-6所描述的2對1多工器)

```
begin
```

```
    TS = 1; TA = 0; TB = 1;
```

```
    #10 TA = 1; TB = 0;
```

```
    #10 TS = 0;
```

```
    #10 TA = 0; TB = 1;
```

```
end
```

HDL 範例 4-9

(測試範例4-6所描述的2對1多工器)

initial

```
$monitor("select = %b A = %b  
B = %b OUT = %b time = %0d",  
TS, TA, TB, Y, $time);
```

endmodule

HDL 範例 4-9

(測試範例4-6所描述的2對1多工器)

```
//Dataflow description of 2-to-1-line  
multiplexer
```

```
//from Example 4-6
```

```
module mux2x1_df (A,B,select,OUT);
```

```
  input  A,B,select;
```

```
  output OUT;
```

```
  assign OUT = select ? A : B;
```

```
endmodule
```

HDL 範例 4-9

(測試範例4-6所描述的2對1多工器)

Simulation log:

select = 1 A=0 B=1 OUT=0 time=0

select = 1 A=1 B=0 OUT=1 time=10

select = 0 A=1 B=0 OUT=0 time=20

select = 0 A=0 B=1 OUT=1 time=30

HDL 範例 4-10

(全加法器之多階電路的閘階層描述)

//Gate-level description of circuit of Fig.
4-2

```
module analysis (A,B,C,F1,F2);  
  input  A,B,C;  
  output F1,F2;  
  wire   T1,T2,T3,F2not,E1,E2,E3;  
  or    g1 (T1,A,B,C);  
  and   g2 (T2,A,B,C);
```

HDL 範例 4-10

(全加法器之多階電路的閘階層描述)

```
and g3 (E1,A,B);  
and g4 (E2,A,C);  
and g5 (E3,B,C);  
or g6 (F2,E1,E2,E3);  
not g7 (F2not,F2);  
and g8 (T3,T1,F2not);  
or g9 (F1,T2,T3);  
endmodule
```

HDL 範例 4-10

(全加法器之多階電路的闡階層描述)

//Stimulus to analyze the circuit

```
module test_circuit;
```

```
    reg [2:0]D;
```

```
    wire F1,F2;
```

```
    analysis fig42(D[2],D[1],D[0],F1,F2);
```

```
    initial
```

```
        begin
```

HDL 範例 4-10

(全加法器之多階電路的閘階層描述)

```
D = 3'b000;
```

```
repeat(7)
```

```
    #10 D = D + 1'b1;
```

```
end
```

```
initial
```

```
    $monitor ("ABC = %b F1 = %b F2  
= %b ",
```

```
                D, F1, F2);
```

```
endmodule
```

HDL 範例 4-10

(全加法器之多階電路的閘階層描述)

Simulation log:

ABC=000 F1=0 F2=0

ABC=001 F1=1 F2=0

ABC=010 F1=1 F2=0

ABC=011 F1=0 F2=1

ABC=100 F1=1 F2=0

ABC=101 F1=0 F2=1

ABC=110 F1=0 F2=1

ABC=111 F1=1 F2=1
