 


D latch



(a) Logic diagram

C	D	Next state of Q
0	X	No change
1	0	Q = 0; Reset state
1	1	Q = 1; Set state

(b) Function table


Fig. 5-6 D Latch

```
module D_latch(Q,D,control);  
    output Q;  
    input D,control;  
    reg Q;  
    always @(control or D)  
        if (control) Q=D;  
endmodule
```


D flip-flop

- module DFF(Q,D,CLK,RST);
- module DFF(Q,D,CLK);
- output Q;
- output RST;
- input D,CLK;
- reg Q;
- always @(posedge CLK or negedge RST)
- always @(posedge CLK)
- if (~RST)
- Q=1'b0;
- else
- Q=D;
- endmodule


$$Q(t + 1) = D$$

 

T flip-flop from D flip-flop and gate

 

 - module TFF(Q,T,CLK,RST); $D = T \oplus Q = TQ' + TQ$
- output Q;
- input T,CLK,RST;
- wire DT;
- assign DT=Q^T;
- DFF TF1(Q,DT,CLK,RST);



(b) From D flip-flop




JK flip-flop from D flip-flop and gate



- module JKFF (Q,J,K,CLK,RST);
- output Q;
- input J,K,CLK,RST;
- wire JK;
- assign JK $= (J \& \sim Q) | (\sim K \& Q)$;
- DFF JK1 (Q,JK,CLK,RST);
- endmodule

$$Q(t+1) = JQ' + K'Q$$

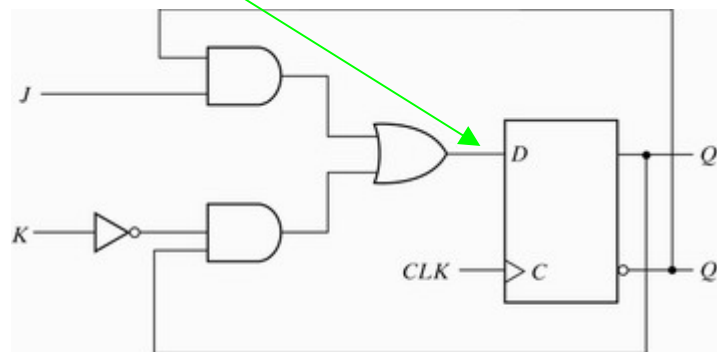


(a) Circuit diagram



- module JK_FF (J,K,CLK,Q,Qnot)
- output Q,Qnot;
- input J,K,CLK;
- reg Q;
- assign Qnot = ~Q;
- always @(posedge CLK)
- case ({J,K})
- 2'b00:Q=Q;
- 2'b01:Q=1'b0;
- 2'b10:Q=1'b1;
- 2'b11:Q=~Q;
- endcase
- endmodule

J	K	Q(t+1)
0	0	Q(t)
0	1	0
1	0	1
1	1	~Q(t)

 

Mealy state diagram



- module mealy_mdl (x,y,CLK,RST);
- input x,CLK,RST;
- output y;
- reg y;
- reg [1:0] Prstate,Nxtstate;
- parameter s0=2'b00, s1=2'b01,
- s2=2'b10, s3=2'b11;
- always @ (posedge CLK or negedge RST)
- if (~RST) Prstate =s0;
- else Prstate =Nxtstate;
-


 


Fig. 5-16 State Diagram of the Circuit of Fig. 5-15

 



- always @ (Prstate or x)
- case (Prstate)
- s0: if (x) Nxtstate=S1;
- else Nxtstate=S0;
- s1: if (x) Nxtstate=S3;
- else Nxtstate=S0;
- s2: if (~x) Nxtstate=S0;
- else Nxtstate=S2;
- s3: if (x) Nxtstate=S2;
- else Nxtstate=S0;

endcase

- always @ (Prstate or x)

case (Prstate)

- s0: y=0;
- s1: if (x) y=1'b0; else y=1'b1;
- s2: if (x) y=1'b0; else y=1'b1;
- s3: if (x) y=1'b0; else y=1'b1;

endcase

- endmodule

 


Fig. 5-16 State Diagram of the Circuit of Fig. 5-15





```
module Moore_mdl (x,ab,CLK,RST);  
input x,CLK,RST;  
output [1:0] ab;  
reg [1:0] state ;  
parameter s0=2'b00,s1=2'b01,s2=2'b10,s3=2'b11;  
always @ (posedge CLK or negedge RST)  
    if (~RST) state =s0;  
    else  
        case (state)  
            s0: if(~x) state =s1; else state =s0;  
            s1: if(x) state =s2; else state =s3;  
            s2: if(~x) state =s3; else state =s2;  
            s3: if(~x) state =s0; else state =s3;  
        endcase  
    assign ab=state  
endmodule
```


 


Fig. 5-19 State Diagram of the Circuit of Fig. 5-18

 

- module Tcircuit (x,y,A,B,CLK,RST)
- input x,CLK,RST;
- output y,A,B;
- wire TA,TB;
- // Flip-flip input equations
- assign TA=x&B;
- assign TB=x;
- // Flip-flip output equations
- assign y=A&B;
- //Instantiate T flip-flip
- T_FF BF (B,TB,CLK,RST)
- T_FF AF (A,TA,CLK,RST)
- endmodule



```

module T_FF(Q,T,CLK,RST);
  output Q;
  input T,CLK,RST;
  reg Q;
  always @ (posedge CLK or negedge RST)
    if (~RST) Q=1'b0;
    else Q=Q^T;
endmodule

```



$$Q(t+1) = T \oplus Q = TQ' + T'Q$$



```

• module testTcircuit;
•   reg x,CLK,RST;
•   wire y,A,B;
•   Tcircuit TC(x,y,A,B,CLK,RST) ;
•   initial
•     begin
•       RST=0;
•       CLK=0;
•       #5 RST=1;
•       repeat(16);
•         #5 CLK=~CLK;
•     end
•   initial
•     begin
•       x=0;
•       #15 x=1;
•       repeat(8);
•         #5 x=~x;
•     end
• endmodule

```

